

#Jenny



Finally I get this ebook, thanks for all these I can get now!

#Rio



Cool! I'am really happy

#Markus Jensen



I did not think that this would work, my best friend showed me this website, and it does! I get my most wanted eBook

#Hun Tsu



wtf this great ebook for free?!

#Che Salsa



My friends are so mad that they do not know how I have all the high quality ebook which they do not!

#Diego Butler



so many fake sites. this is the first one which worked! Many thanks

**Electrical circuit components**

Name: \_\_\_\_\_

Electricity is a 'secondary' source of energy. In other words, other sources of energy are needed to produce electricity. Name three other sources of electricity.

1. \_\_\_\_\_ 2. \_\_\_\_\_ 3. \_\_\_\_\_

An electric circuit is like a **pathway** made of wires that electrons can flow through.

The word 'circuit' sounds like 'circle', and a circuit needs to be circular in order to work.

Electricity always **flows** in a circuit from the negative pole of a battery to its positive pole. The flow of electricity creates an electric current.

An electric circuit needs two main things in order to work:

- A **power source**.
- To be **complete**.





This means that the wires connecting all the objects (switches, light-bulbs, buzzers and so on) must start and end at the power source before the circuit can work. That's why batteries have a top and bottom (+ and -) so that they can carry the charge all the way around a circuit.

A battery or other **power source** gives the force (voltage) that makes the electrons move. When the electrons get to a device like a light bulb, your computer, or a refrigerator, they give it the power to work.

A load is a device that uses electricity (like a buzzer or a light bulb). The load needs electrical energy to be able work.

Many circuits have a **switch** so that they can be turned on and off. When the switch is off, it makes a gap in the circuit and the electrons are not able to flow around. When the switch is turned on, it closes the gap and the electricity is able to move and make the device work.

Study the pictures of circuits below. Identify the circuits which will allow the bulbs to shine. Use a ✓ to show your selection.

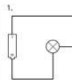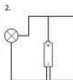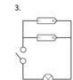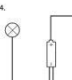1.  2.  3.  4. 

© 4 Classroom 2015 [www.4classroom.co.za](http://www.4classroom.co.za)

[Download PDF version of :](#)  
**Conceptual Physics 34 Electric Current Answers**